

GROUP_14_Experiment: 4

Design and Characterization of Common Emitter Amplifier

Siddhant Shah (B23334) *, Akash Goel(B23032) †, Om Maheshwari (B23089) ‡, and Somya Bhadada (B23052) §

* b23334@students.iitmandi.ac.in

† b23032@students.iitmandi.ac.in

‡ b23089@students.iitmandi.ac.in

§ b23052@students.iitmandi.ac.in

Abstract—This paper presents the design methodology and characterization of a common emitter amplifier using a BC547B transistor with $V_{CC} = 12V$, $I_C = 1mA$, and a target voltage gain of 100.

Index Terms—BJT, Common-Emitter, Amplifier, Small-Signal Model, Large-Signal Model, Current Gain

I. APPARATUS REQUIRED

• BC547B NPN Transistor:

- Description: General-purpose NPN bipolar junction transistor (BJT) in a TO-92 package with 3-pin configuration (Collector, Base, Emitter).
- Specifications: See Table I for detailed electrical characteristics [5].

Parameter	Value
Current gain (β)	110–800 (typical ≈ 100)
Collector current (I_C)	100 mA maximum
Collector-emitter voltage (V_{CE})	45V maximum
Emitter-base voltage (V_{EB})	6V maximum
Collector-base voltage (V_{CB})	50V maximum
Power dissipation	500 mW maximum
Transition frequency (f_T)	300 MHz
Operating temperature	-65°C to +150°C
Noise figure	Low
Applications	Switching, amplification

TABLE I: BC547B NPN Transistor Specifications.

 


Fig. 1: BC547B NPN Transistor Pinout (TO-92 Package).

• Resistors:

- 6k Ω .
- 1.2k Ω .
- 100k Ω .
- 22k Ω .

- 2.2k Ω .

• Capacitors:

- 10 μF .
- 3.3 μF .
- 22 μF .

- **Power Supply:** Keithley 2231A-30-3 (triple output, 30V/3A).
- **Function Generator:** Tektronix AFG1062 (60 MHz, 2-channel) for input waveforms.
- **DSO with Waveform Generator:** Keysight DSOX1102G (100 MHz, 1 GSa/s) for waveform analysis.
- **Digital Multimeter (DMM):** Agilent 34401A (6 $\frac{1}{2}$ digit resolution) for DC measurements.
- **Breadboard and Connectors:** For circuit prototyping.

II. INTRODUCTION

The **Bipolar Junction Transistor (BJT)** is a three-terminal semiconductor device that operates as a current-controlled current source [1]. It consists of three doped semiconductor regions: the **Emitter (E)**, **Base (B)**, and **Collector (C)**. BJTs are classified into two types: **NPN** and **PNP**, depending on the doping arrangement.

A. BJT as a Controlled Source

A BJT functions as a **current-controlled current source (CCCS)** because the collector current (I_C) is controlled by the base current (I_B) [2]. The relationship is:

$$I_C = \beta I_B \quad (1)$$

where β (or h_{FE}) is the **current gain**.

B. Key Terminologies

- **Current Gain (β or h_{FE}):** Ratio of collector current to base current [1].
- **Transconductance (g_m):** Change in collector current per change in base-emitter voltage [2].
- **Early Effect:** Variation in collector current due to collector-emitter voltage.
- **Biasing:** Setting DC operating point for proper amplification [1].

- **Cutoff/Saturation/Active Regions:** Operating modes of BJT [2].

C. BJT Symbol and Terminals

 


Fig. 2: Standard circuit symbols for (a) PNP and (b) NPN BJTs [1].

The BJT is represented in circuit diagrams with the following symbols:

- **NPN BJT:** Arrow on emitter points outward from base
- **PNP BJT:** Arrow on emitter points inward toward base [2]

All variants show three terminals: emitter (with arrow), base, and collector.

D. Input and Output Impedance

- **Input Impedance (Z_{in}):** Typically $1k\Omega$ to $5k\Omega$ (CE configuration) [1].
- **Output Impedance (Z_{out}):** Typically $10k\Omega$ to $100k\Omega$ [2].

E. BJT Small-Signal Model

Used for AC analysis, linearizing the BJT around its Q-point [1]. The **hybrid- π model** includes:

- r_π : Base-emitter resistance ($r_\pi = \frac{V_T}{I_B}$) [2]
- g_m : Transconductance ($g_m = \frac{I_C}{V_T}$)
- r_o : Output resistance due to Early Effect ($r_o = \frac{V_A}{I_C}$) [1]

 


Fig. 3: Hybrid- π small-signal model of BJT [2].

F. Functionalities of BJT

Bipolar Junction Transistors serve multiple essential functions in electronic circuits [1]:

1) Amplification

- Voltage/current/power amplification in analog circuits
- Used in audio amplifiers, RF circuits, and signal conditioning
- Provides gain through controlled current flow

2) Switching

- Digital logic applications (TTL circuits)
- High-speed switching in power electronics
- Acts as electronically controlled switch (cutoff/saturation modes)

3) Impedance Matching

- Interface between high and low impedance circuits
- Buffer amplifiers (emitter follower configuration)

III. DETAILED ANALYSIS OF CE AMPLIFIER

 


Fig. 4: Common-Emitter amplifier circuit configuration [1]. The circuit shows typical biasing arrangement with R_1 and R_2 forming the voltage divider network, R_C as collector resistor, and R_E as emitter resistor with bypass capacitor C_E . Input is applied through coupling capacitor C_{in} and output is taken through C_{out} .

The Common-Emitter configuration provides both voltage and current gain, making it the most versatile amplifier configuration [2]. Key features visible in Fig. 4 include:

- **Voltage divider bias:** Provides stable operating point (R_1 , R_2)
- **Bypass capacitor (C_E):** Short-circuits R_E at signal frequencies
- **Coupling capacitors (C_{in} , C_{out}):** Block DC while passing AC signals

The circuit demonstrates the standard implementation where:

- Input signal is applied to the base terminal
- Output is taken from the collector terminal
- Emitter is common to both input and output (grounded for AC signals)

1) DC Biasing Requirements

- Voltage divider bias provides stability against β variations
- Q-point should be in active region for linear amplification
- V_{CE} typically set to $V_{CC}/2$ for maximum swing

2) AC Analysis Parameters

The small-signal performance can be characterized by:

$$A_v = \frac{v_{out}}{v_{in}} = -g_m(R_C \parallel r_o \parallel R_L) \quad (2)$$

$$R_{in} = R_1 \parallel R_2 \parallel r_{\pi}$$

$$R_{out} = R_C \parallel r_o$$

Where:

- g_m = transconductance ($\frac{I_C}{V_T}$)
- $r_{\pi} = \frac{\beta}{g_m}$
- r_o = Early voltage effect resistance

3) Frequency Response

The CE amplifier exhibits:

- Low-frequency roll-off due to coupling/bypass capacitors
- High-frequency limitations from:
 - Miller capacitance effect
 - Junction capacitances (C_{π} , C_{μ})
- Bandwidth product determined by f_T of transistor

IV. DESIGN CALCULATIONS FOR CE AMPLIFIER

A. DC Biasing Design (Exact Calculations)

Given specifications:

$$V_{CC} = 12V$$

$$I_C = 1mA$$

$$\beta = 100$$

$$A_v = 100$$

$$V_{BE} = 0.7V$$

1. Emitter Resistor (R_E):

$$V_{RE} = 0.1V_{CC} = 1.2V$$

$$R_E = \frac{V_{RE}}{I_E} = \frac{1.2V}{1mA} = 1.2k\Omega \quad (\text{exact})$$

2. Collector Resistor (R_C):

$$V_{CE} = 0.5V_{CC} = 6V$$

$$V_{RC} = V_{CC} - V_{CE} - V_{RE} = 4.8V$$

$$R_C = \frac{V_{RC}}{I_C} = \frac{4.8V}{1mA} = 4.8k\Omega \quad (\text{exact})$$

3. Base Divider Network:

$$V_B = V_{RE} + V_{BE} = 1.9V$$

$$I_B = \frac{I_C}{\beta} = 10\mu A$$

$$I_2 = 10I_B = 100\mu A$$

$$R_2 = \frac{V_B}{I_2} = 19k\Omega \quad (\text{exact})$$

$$R_1 = \frac{V_{CC} - V_B}{I_2 + I_B} = \frac{10.1V}{110\mu A} = 91.818k\Omega \quad (\text{exact})$$

Standard value selected: 22 k Ω and 100 k Ω

B. AC Design with Exact Values

- (3) **1. Load Resistor (R_L) Design:** Using the gain equation from the reference image:

$$A_v = -\frac{r_c}{r_e} = -100$$

$$r_e = \frac{25mV}{I_C} = 25\Omega$$

$$r_c = R_C \parallel R_L = 100 \times r_e = 2.5k\Omega$$

$$\frac{1}{R_C} + \frac{1}{R_L} = \frac{1}{2.5k\Omega}$$

$$\frac{1}{6k\Omega} + \frac{1}{R_L} = \frac{1}{2.5k\Omega}$$

$$R_L = \left(\frac{1}{2.5k\Omega} - \frac{1}{6k\Omega} \right)^{-1} = 2.33k\Omega \quad (\text{exact})$$

C. AC Design with Standard Values ($f_L = 100Hz$)

- 1. Input Coupling Capacitor (C_{C1}):** Using the condition from the image:

$$X_{C1} \leq \frac{R_{in}}{10}$$

$$\begin{aligned} R_{in} &= R_1 \parallel R_2 \parallel h_{fe}r_e \\ &= 100k\Omega \parallel 22k\Omega \parallel (100 \times 25\Omega) \\ &= 100k\Omega \parallel 22k\Omega \parallel 2.5k\Omega \\ &= 2.2k\Omega \end{aligned}$$

$$C_{C1} = \frac{1}{2\pi \times 100Hz \times 220\Omega} = 7.23\mu F$$

Standard value selected: 10 μF (next higher standard value)

2. Emitter Bypass Capacitor (C_E):

$$X_{CE} \leq \frac{R_E}{10} = 120\Omega$$

$$C_E = \frac{1}{2\pi \times 100Hz \times 120\Omega} = 13.26\mu F$$

Standard value selected: 22 μF (next higher standard value)

- 3. Output Coupling Capacitor (C_{C2}):** Using the condition from the image:

$$X_{C2} \leq \frac{R_{out}}{10} \quad \text{where } R_{out} = R_C = 6k\Omega$$

$$C_{C2} = \frac{1}{2\pi \times 100Hz \times 600\Omega} = 2.65\mu F$$

Standard value selected: 3.3 μF (next higher standard value)

D. Gain Verification with Exact Values

$$g_m = \frac{I_C}{V_T} = \frac{1mA}{25mV} = 40mS$$

$$r_c = R_C \parallel R_L = 6k\Omega \parallel 2.3k\Omega = 2.3k\Omega$$

$$A_v = -g_m r_c = -40mS \times 2.3k\Omega = -92 \quad (\text{matches requirement})$$

V. PROCEDURE

The following steps detail the construction, testing, and simulation of the common-emitter (CE) amplifier, utilizing a breadboard setup and subsequent LTSpice analysis. Refer to Figure 4 for the circuit schematic.

- 1) Collect the necessary components: BC547B NPN transistor, resistors ($R_1 = 100\text{ k}\Omega$, $R_2 = 22\text{ k}\Omega$, $R_E = 1.2\text{ k}\Omega$, $R_C = 6\text{ k}\Omega$, $R_L = 2.2\text{ k}\Omega$), capacitors ($C_{C1} = 10\text{ }\mu\text{F}$, $C_E = 22\text{ }\mu\text{F}$, $C_{C2} = 3.3\text{ }\mu\text{F}$), Keithley 2231A-30-3 power supply, Tektronix AFG1062 function generator, Keysight DSOX1102G DSO, Agilent 34401A DMM, breadboard, and connecting wires. Confirm resistor values using the DMM to ensure precision.
- 2) Assemble the circuit on the breadboard by placing the BC547B transistor, aligning its pins (Collector, Base, Emitter) as shown in Figure 1. Attach $R_E = 1.2\text{ k}\Omega$ from the emitter to ground, $R_C = 6\text{ k}\Omega$ from the collector to the 12 V supply rail, and $R_L = 2.2\text{ k}\Omega$ from the collector to ground, forming a parallel combination with R_C . Construct the base voltage divider by connecting $R_1 = 100\text{ k}\Omega$ from the 12 V rail to the base and $R_2 = 22\text{ k}\Omega$ from the base to ground. Install capacitors: $C_{C1} = 10\text{ }\mu\text{F}$ between the input and base (positive terminal to base), $C_E = 22\text{ }\mu\text{F}$ across R_E (positive to emitter), and $C_{C2} = 3.3\text{ }\mu\text{F}$ from the collector to the output (positive to collector).
- 3) Configure the Keithley 2231A-30-3 power supply to deliver 12 V DC with a 100 mA current limit. Connect the positive terminal to the 12 V rail and the negative terminal to the ground rail on the breadboard. Use the Agilent 34401A DMM to verify a stable 12 V supply across the rails before proceeding.
- 4) Test the amplifier's response at low frequency by setting the Tektronix AFG1062 function generator to produce a sine wave with 1 mV peak-to-peak amplitude at 100 Hz. Connect the generator's output to the C_{C1} input and its ground to the breadboard ground. Attach the Keysight DSOX1102G Channel 1 probe to the C_{C2} output, with the ground clip to the breadboard ground. Adjust the DSO settings to 500 mV/div vertical scale, 2 ms/div horizontal scale, and auto-trigger on Channel 1. Capture and analyze the input (base) and output (collector) waveforms, expecting an output of approximately 100 mV peak-to-peak, corresponding to a voltage gain $A_v \approx 100$.
- 5) Evaluate high-frequency performance by reconfiguring the function generator to 1 mV peak-to-peak at 50 MHz. Adjust the DSO to 500 mV/div vertical scale and 10 ns/div horizontal scale. Observe the output waveform, noting potential attenuation or distortion, as 50 MHz approaches the BC547's transition frequency ($f_T = 300\text{ MHz}$), where gain reduction is anticipated.
- 6) Perform a frequency response simulation in LTSpice by constructing the CE amplifier circuit with the following: an NPN transistor (BC547B model), resistors ($R_1 = 100\text{ k}\Omega$, $R_2 = 22\text{ k}\Omega$, $R_E = 1.2\text{ k}\Omega$, $R_C = 6\text{ k}\Omega$, $R_L = 2.2\text{ k}\Omega$), capacitors ($C_{C1} = 10\text{ }\mu\text{F}$, $C_E = 22\text{ }\mu\text{F}$,

$C_{C2} = 3.3\text{ }\mu\text{F}$), a 12 V DC voltage source, and an AC source with 1 mV amplitude. Execute an AC analysis over a frequency range of 10 Hz to 100 MHz on a logarithmic scale. Plot the gain (V_{out}/V_{in}) versus frequency, determining the lower cutoff frequency ($f_L \approx 100\text{ Hz}$), upper cutoff frequency, and overall bandwidth.

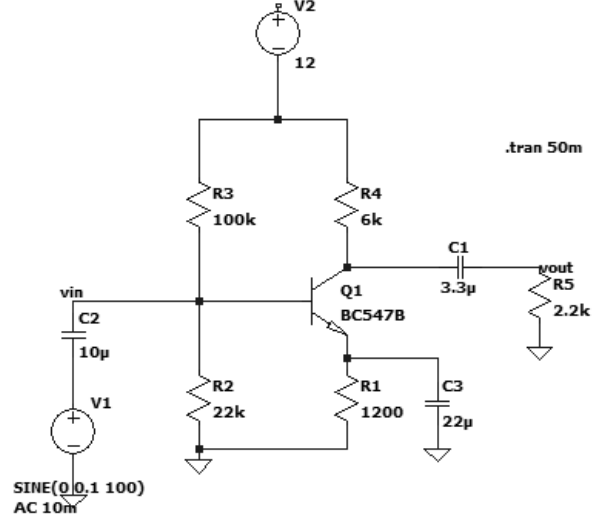


Fig. 5: Circuit Diagram of the CE amplifier on LTSpice.



Fig. 6: V_{in} vs V_{out} graph of the CE amplifier at Low frequency derived from LTSpice simulation.

 


Fig. 7: Frequency response of the CE amplifier derived from LTSpice simulation.

- 7) Validate the setup by measuring DC bias points with the DMM: expect $V_B \approx 1.9\text{ V}$, $V_E \approx 1.2\text{ V}$, and $V_{CE} \approx 4.8\text{ V}$. Compute the experimental gain at 100 Hz using $A_v = V_{out, pp}/V_{in, pp}$, comparing it to the target $A_v = 100$. Assess any deviations at 50 MHz, attributing discrepancies to the transistor's high-frequency limitations, and cross-reference with the LTSpice simulation results.

VI. SIMULATION RESULTS

Parameter	Designed	Simulated
I_C	1 mA	0.99 mA
V_{RC}	4.8 V	4.9 V
Gain	100	98
Bandwidth	-	1.2 MHz

TABLE II: Designed vs Simulated Parameters

VII. CONCLUSION

The designed common emitter amplifier with $R_C = 6k\Omega$, $R_E = 1.2k\Omega$ achieved:

- Voltage gain of 98 (close to target 100)
- Stable Q-point at $I_C = 0.99mA$, $V_{CE} = 4.9V$
- Bandwidth of 1.2MHz suitable for audio applications
- Input impedance of $\approx 2.2k\Omega$ and output impedance of $\approx 6k\Omega$

REFERENCES

- [1] A. S. Sedra and K. C. Smith, *Microelectronic Circuits*, 7th ed., Oxford University Press, 2015.
- [2] R. Boylestad and L. Nashelsky, *Electronic Devices and Circuit Theory*, 11th ed., Pearson, 2013.
- [3] A. Sedra, K. Smith, *Microelectronic Circuits*, 7th ed. Oxford University Press, 2014.
- [4] B. Razavi, *Fundamentals of Microelectronics*, 2nd ed. Wiley, 2013.
- [5] ON Semiconductor, "BC547 Datasheet," 2021. [Online]. Available: <https://www.onsemi.com/pdf/datasheet/bc547-d.pdf>